

<http://onsemi.com>

The oscillator section consists of two current sources; one charging, the other discharging the timing capacitor C_T , between two fixed voltage levels. The levels are approximately 500 mV apart. The ratio between the charge

current and the discharge current is set within the controller to be 1:6. This ratio creates a fixed duty cycle D_{MAX} of 6/7 or 0.86. Typical operating waveforms, including the timing ramp C_T , are illustrated in Figure 2.

 


Figure 2. Typical Operating Waveform

This versatile controller can be configured for buck, boost, buck-boost and also inverting applications. For detailed information regarding controller operation refer to the NCP3063 data sheet. The essentials of the control method can be observed in the waveforms of Figure 2. The output voltage is fed back to the inverting input (Pin 5) of the comparator (Figure 1) via a resistor divider. If the output is above or below the setpoint, the comparator “gates” a series of clock cycles through the power switch. Control of the output voltage is achieved by varying the average number of “on cycles” to the number of “off cycles” in a given time interval.

The transfer functions (or gain) V_{OUT}/V_{IN} for buck, boost and buck-boost operation, neglecting circuit losses, are given by the following equations:

$$\text{Buck Transfer Function} = D \quad (\text{eq. 1})$$

$$\text{Boost Transfer Function} = \frac{1}{(1 - D)} \quad (\text{eq. 2})$$

$$\text{Buck-Boost Transfer Function} = \frac{D}{(1 - D)} \quad (\text{eq. 3})$$

If the value D_{MAX} equal to 0.86 is inserted into the above equations, the maximum gain available for each topology is determined.

Maximum buck gain = 0.86

Maximum boost gain = 7.14

Maximum buck-boost gain = 6.14

The maximum gain values indicated above may be considerably more than a particular application requires. For example a 12 V to 5 V buck application requires a gain of

0.42 and a corresponding $D = 0.42$, a 12 V to 19 V boost application requires a gain of 1.58 resulting in a nominal $D = 0.37$, while a 12 V to 12 V buck-boost application requires unity gain and $D = 0.5$. Hence dependent on the application, the ratio of “on pulses” to “off pulses” can be very large or very small, to maintain output regulation against a given set point. In turn, this may result increased output ripple, requiring a large output capacitor. In extreme cases, audible noise generation is possible, if the pulse repetition rate is in the audio band.

The addition of a feedforward resistor can help to alleviate these issues. The ramp circuit is modified as illustrated in Figure 3 by the addition of an external current source I_{FF} at the C_T pin. This current source, in the simplest case, is created by adding a resistor between V_{IN} and C_T .

 


Figure 3.

Adding an external current will reduce the time it takes to charge the C_T capacitor between the ramp's minimum and maximum thresholds. The design equations relating to the oscillator section are given below.

$$T_{ON} = C_T * V_{RAMP} / \sum I_{CHARGE} \quad (\text{eq. 4})$$

$$T_{OFF} = C_T * V_{RAMP} / \sum I_{DISCHARGE} \quad (\text{eq. 5})$$

$$T_S = (T_{ON} + T_{OFF}) \quad (\text{eq. 6})$$

$$D_{MOD} = \frac{T_{ON}}{T_{OFF}} \quad (\text{eq. 7})$$

$$F_S = \frac{1}{T_S} \quad (\text{eq. 8})$$

Table 1 shows the corresponding reduction in duty cycle D_{MOD} as a normalized function of the charging and discharging currents flowing into the timing capacitor C_T . The table also shows the change in normalized oscillator frequency.

Once an optimum duty cycle has been identified and I_{FF} selected, the value of C_T can be ratio metrically adjusted to set the design frequency. Once set, the frequency variation against duty cycle is small over a wide range of external charging currents.

Table 1. VARIATION OF DUTY CYCLE D_{MOD} AND FREQUENCY F_{MOD} AS A FUNCTION OF NORMALIZED EXTERNAL CURRENT, CHARGING THE TIMING CAPACITOR C_T .

External Charging Current	Internal Charging Current	Internal Discharging Current	Duty Cycle D_{MOD}	Frequency F_{MOD}
0	1	6	0.86	1.00
1	1	5	0.71	1.43
2	1	4	0.66	1.71
3	1	3	0.50	1.71
4	1	2	0.29	1.43
5	1	1	0.14	0.86

Practical Example

 


Figure 4. Schematic of a Noninverting Buck-Boost Topology

Figure 4 is a schematic of a noninverting buck-boost topology. The input is a nominal 12 V_{IN} while the output is regulated to 12 V_{OUT} . Assuming no circuit losses, the transfer function or gain of this application is unity and the duty cycle determined from the buck boost transfer function is 0.5. Referring to Table 1, a 3:1 ratio for the external charging current to internal charging current would generate a modified duty D_{MOD} of 0.5.

However, to accommodate conduction and switching losses in the power components, we will start by selecting a 2:1 ratio, providing a D_{MOD} of 0.66 and modified gain (Equation 3) of 0.66/0.34 or 1.94.

The nominal charge and discharge currents for the NCP3063 are listed below:

- Charging Current is 260 μA @ 5 V V_{CC} / 25°C and 280 μA @ 40 V V_{CC} / 25°C.
- Discharging Current is 1550 μA @ 5 V V_{CC} / 25°C and 1700 μA @ 40 V V_{CC} / 25°C.

The data above may be verified from measurements of the C_T ramp illustrated in Figure 5 before inserting the feedforward resistor R3 in Figure 4.

 


Figure 5. Ramp Waveform
 $C_T = 1800 \text{ pF}$, $T_S = 4.94 \text{ } \mu S$

Rearranging Equation 4, the charge current I_{CHARGE} is given by the expression

$$I_{CHARGE} = C_T * \Delta V_{RAMP} / T_{ON} \quad (\text{eq. 9})$$

Substituting the measured values taken from the ramp waveform in Figure 5 into Equation 9, $I_{CHARGE} = 1800 \text{ pF} * 628 \text{ mV} / 4.18 \text{ } \mu\text{S} = 270 \text{ } \mu\text{A}$ which corresponds to the data above.

For D_{MOD} of 0.66, we require an external current of $520 \text{ } \mu\text{A}$. The average ramp voltage from Figure 5 is 0.9 V and V_{IN} is nominally 12 V , hence the value of the feedforward resistor $R3$ may be determined from the expression $(12 \text{ V} - 0.9 \text{ V}) / 520 \text{ } \mu\text{A}$ or $21.3 \text{ k}\Omega$. A preferred value of $20 \text{ k}\Omega$ is selected; I_{FF} is then $555 \text{ } \mu\text{A}$.

$$\sum I_{CHARGE} = 555 \text{ } \mu\text{A} + 270 \text{ } \mu\text{A} = 0.825 \text{ mA}$$

$$\sum I_{DISCHARGE} = 1550 \text{ } \mu\text{A} - 555 \text{ } \mu\text{A} = 0.995 \text{ mA}$$

From Table 1, it is apparent that in order to maintain the same switching frequency F_S after an external current source is added in circuit, the value of the timing capacitor C_T has to be increased by a design factor 1.72 times. Here C_T was increased to 3.9 nF .

$$C_T * \Delta V_{RAMP} = 3.9 \text{ nF} * 560 \text{ mV} = 2.18 \cdot 10^{-9}$$

Substituting the values above into Equations 4 and 5 gives:


$$T_{ON} = 2.64 \text{ } \mu\text{S} \quad T_{OFF} = 2.19 \text{ } \mu\text{S}$$

$$T_S = (T_{ON} + T_{OFF}) = 4.83 \text{ } \mu\text{S}$$

$$D_{MOD} = \frac{T_{ON}}{T_S} = 0.547$$

$$F_S = \frac{1}{T_S} = 207 \text{ kHz}$$

The modified ramp is captured in Figure 6.

 

**Figure 6. Modified Ramp Waveform,
 $C_T = 3.9 \text{ nF}$, $I_{FF} = 555 \text{ } \mu\text{A}$**


Data measured from the ramp waveform in Figure 6 is given below and shows good correlation with the calculated results above.

$$T_{ON} = 2.68 \text{ } \mu\text{S} \quad T_{OFF} = 2.28 \text{ } \mu\text{S}$$

$$T_S = (T_{ON} + T_{OFF}) = 4.96 \text{ } \mu\text{S}$$

$$D_{MOD} = \frac{T_{ON}}{T_{OFF}} = 0.54$$


$$F_S = \frac{1}{T_S} = 202 \text{ kHz}$$

 

**Figure 7. Buck-Boost Output Ripple with
Voltage Feedforward Applied**

The output ripple across a $33 \text{ } \mu\text{F}$ electrolytic and $20 \text{ } \mu\text{F}$ MLCC capacitors in parallel is shown in Figure 7. The output voltage is regulated at 11.9 V . The ripple is 70 mV peak to peak with a repetition rate around 9 kHz .

The collector waveform of the NPN transistor Q2 and modified C_T ramp are illustrated in Figure 8. It is observed that energy is flowing from primary to secondary for many switching cycles to support the 100 mA output load. The converter was then operated without feedforward at the same switching frequency. The output capacitor bank and the load were identical. The output ripple is shown in Figure 9.

 

**Figure 8. Collector Waveform Q2 with
Modified Ramp D_{MOD}**

 


Figure 9. Buck Boost Output Ripple Without Feedforward Applied

It is evident that the output ripple has increased to 1.2 V peak-to-peak with a repetition rate around 3 kHz and the higher ripple of the output waveform results in the average output voltage being regulated at 12.3 V.

 


Figure 10. Collector Waveform Q2 with D_{MAX} Ramp

The collector waveform of the NPN transistor Q2 and D_{MAX} ramp is shown in Figure 10. Here it is evident that the energy flow to support the same 100 mA output is drawn from the input in five switching cycles, during which time the voltage on the output capacitor C2 is increased by 1.2 V. C2 is discharged by the output load for several hundred microseconds before the gate oscillator in the NCP3063 restarts.

Conclusion

By summing an external current source into the C_T pin of the NCP3063, it is possible to optimize the open loop gain of buck, boost or buck boost topologies for any given application. Reducing the controller's maximum duty cycle of 0.86 to a lower value D_{MOD} allows the power components to be designed for lower stress. Input capacitors, output capacitors, inductor, switches and diodes can all benefit from the D_{MAX} reduction. The effect of output capacitor ripple was investigated in the particular case of a buck-boost topology. It is evident that a large reduction in output capacitor is possible when a single resistor feedforward function is implemented. This technique can also be applied to the MC33063/MC34063 but be aware that the ramp charge and discharge currents are different.

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5773-3850

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local Sales Representative